
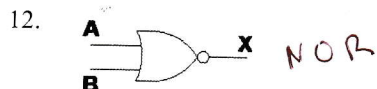
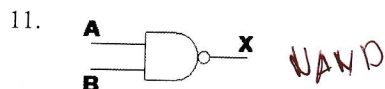
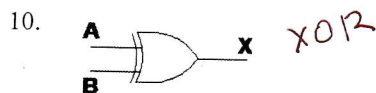
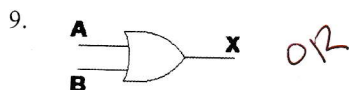
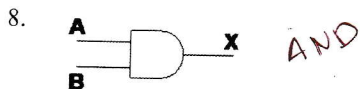


Palomar College
Computer Science &
Information Technology
CSCI 112 Programming Fundamentals I
Homework 5

For Exercises 1 - 12, match the gate with the diagram or description of the operation.

- A. AND
- B. NAND
- C. XOR
- D. OR
- E. NOR
- F. NOT

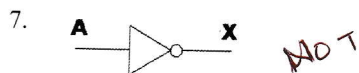1. Inverts its input. *NOT*
2. Produces a 1 only if all its inputs are 1 and a 0 otherwise. ~~NOT~~ *AND*
3. Produces a 0 only if all its inputs are 0 and a 1 otherwise. *OR*
4. Produces a 0 only if its inputs are the same and a 1 otherwise. *XOR*
5. Produces a 0 if all its inputs are all 1 and a 1 otherwise. *NAND*
6. Produces a 1 if all its inputs are 0 and a 0 otherwise. *NOR*



13. What are the three notational methods for describing the behavior of gates and circuits?

booleans, logic diagrams, and truth tables

Palomar College
Computer Science &
Information Technology
CSCI 112 Programming Fundamentals I
Homework 5

14. Name six types of gates.

NOT, AND, OR, XOR, NAND, NOR

15. Give the three representations of a NOT gate and say in words what NOT means.

$$X = A'$$

How its
represented in
code



logic diagram
to represent the
expression

A	X
0	1
1	0

what inputs will
and won't work

16. Give the three representations of an AND gate and say in words what AND means.

$$X = A \cdot B$$

how its
represented
in code



logic diagram
to represent the
expression

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

what inputs will
and won't work

17. Give the three representations of an OR gate and say in words what OR means.

$$X = A + B$$



A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

18. Give the three representations of an XOR gate and say in words what XOR means.

$$X = A \oplus B$$



A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

19. Give the three representations of a NAND gate and say in words what NAND means.

$$X = (A \cdot B)'$$




A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

**Palomar College
Computer Science &
Information Technology
CSCI 112 Programming Fundamentals I
Homework 5**

20. Give the three representations of a NOR gate and say in words what NOR means.

$$X = (A + B)'$$

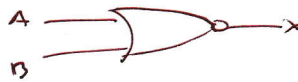

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

21. Compare and contrast the AND gate and the NOR gate.

the out puts are reversed

AND	0	NOR	1
	0		0
	0		0
	1		0

22. Draw and label the symbol for a three input AND gate, then show its behavior with a truth table.




A	B	X	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

23. Draw and label the symbol for a three-input OR gate, then show its behavior with a truth table.




A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

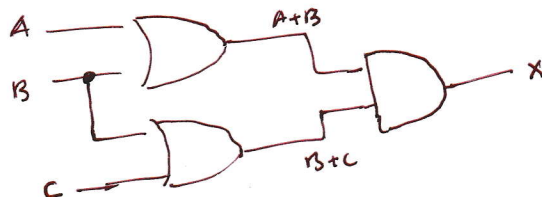24. Draw a circuit diagram corresponding to the following Boolean expression:
 $(A + B)(B + C)$




Palomar College
Computer Science &
Information Technology
CSCI 112 Programming Fundamentals I
Homework 5

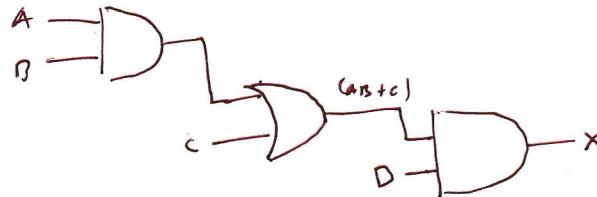
25. Draw a circuit diagram corresponding to the following Boolean expression:
 $(AB + C)D$



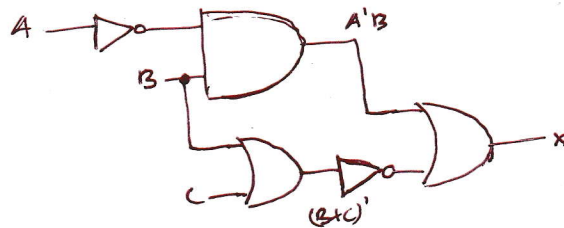
26. Draw a circuit diagram corresponding to the following Boolean expression:
 $A'B + (B+C)'$



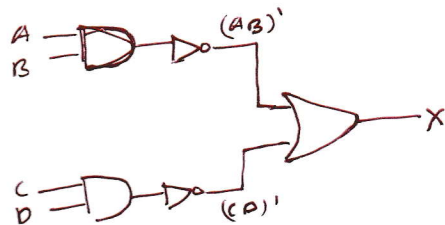27. Draw a circuit diagram corresponding to the following Boolean expression:
 $(AB)' + (CD)'$



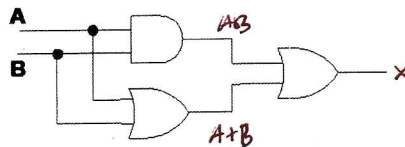
28. Show the behavior of the following circuit with a truth table:



A	B	AB	A+B	X
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	1


Palomar College
Computer Science &
Information Technology
CSCI 112 Programming Fundamentals I
Homework 5

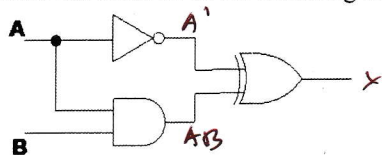29. Show the behavior of the following circuit with a truth table:



A	B	A'	AB	X
0	0	1	0	0
0	1	1	0	1
1	0	0	0	1
1	1	0	1	0

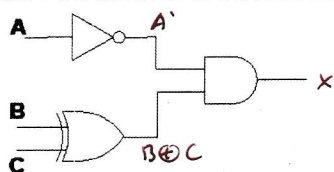
30. Show the behavior of the following circuit with a truth table:



A	B	C	A'	B ⊕ C	X
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	0	0	0

Palomar College
Computer Science &
Information Technology
CSCI 112 Programming Fundamentals I
Homework 5

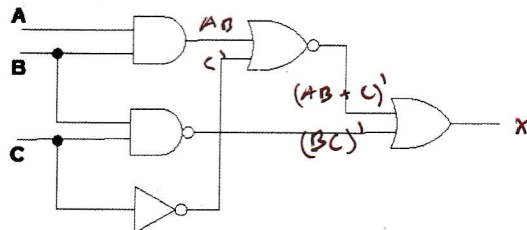31. Show the behavior of the following circuit with a truth table:



BC
0
0
0
0
0
0
1

A	B	C	AB	C'	(AB + C)'	(BC)'	X	X
0	0	0	0	1	1	1	1	1
0	0	1	0	0	1	0	1	1
0	1	0	0	0	1	1	1	1
0	1	1	0	0	1	0	1	1
1	0	0	0	1	1	1	1	1
1	0	1	0	0	1	0	1	1
1	1	0	1	0	0	1	1	1
1	1	1	1	0	0	0	1	1

32. Name six properties of Boolean algebra and explain what each means.

Commutative : $AB = BA$ it equals itself

Associative : $(AB)C = A(BC)$ it equals itself
multiplication

Distributive : $A(B+C) = (AB) + (AC)$ Factoring is possible

Identity : $A1 = A$

multiplied or added
to itself equals
itself

Complement : $(A)A' = 0$ $A + A' = 1$

works like regular
multiplication or addition